

IC-37 CAPACITORS IN CIRCUITS

3/05/2023

FOR IN-CLASS AND TAKE-HOME LAB KIT

37-1 OBJECTIVES

The purpose of this lab is to determine how a capacitor behaves in an R-C circuit by measuring the time for charging and discharging. This will also be done for two capacitors in Series and in Parallel.

37-2 EQUIPMENT

AC/DC Electronics Lab Board

Capacitors

Resistors

Wire Leads

D-cell Battery

Stopwatch / Cellphone

Voltage Sensor / Digital Multimeter (DMM).

Capstone Software.



37-3 THEORY

An RC circuit is one in which we have a resistor in series with a capacitor (Figure 1). In this figure, the battery is not connected to the circuit, and there is no charging of the capacitor. Assume that the capacitor is initially completely un-charged (which can be done by momentarily connecting both ends of the capacitor with a piece of wire). The switch is then thrown to position 'a' at time $t = 0$ s (figure 2). This starts charging the capacitor, and the rate of charging is given by:

$$q(t) = Q \left(1 - e^{-\frac{t}{RC}} \right) \quad (1)$$

Where $q(t)$ is the charge at time t after charging starts, R and C are the values of the resistance and capacitance. Q is the maximum charge that can be stored on the capacitor, and is given by

$$Q = C \Delta V \quad (2)$$

Where C is the Capacitance of the capacitor, and ΔV is the applied potential across the capacitor ($= \mathcal{E}$ volts). The term RC is called the time constant (τ) of the RC circuit, and is the time taken for the capacitor to charge to 63.2% of its maximum possible value.

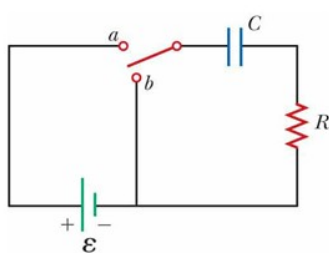


Figure 1

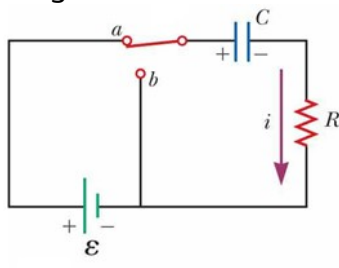


Figure 2

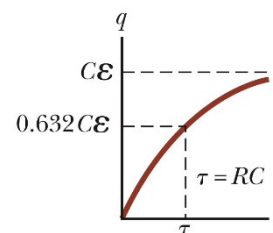


Figure 3

The capacitor charges with time as shown in Figure 3. Even though equation (1) and this curve indicate that the capacitor will never be fully charged, for most practical purposes we consider that the capacitor is fully charged after a time that is more than 5 time-constants have passed.

To discharge the capacitor through the resistor, we move the switch to position 'b', as in Figure 4. The capacitor discharges according to equation (3). The charge decreases exponentially as shown in Figure 5.

$$q(t) = Q e^{\frac{-t}{RC}} \quad (3)$$

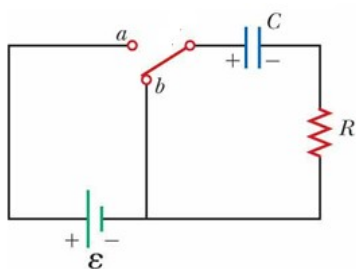


Figure 4

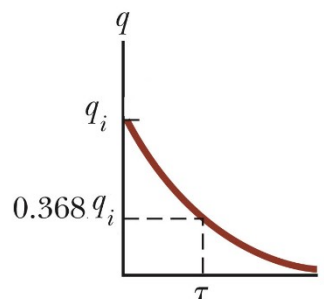


Figure 5

In this experiment we will determine the time that it takes for the capacitor to charge and discharge to some value. Instead of measuring the charge, we will measure the voltage across the capacitor, which is an indicator of how much the capacitor has charged, as a function of the maximum charge. So while charging, when the potential difference across the capacitor reaches the battery potential, the potential drop across the resistor is zero and there is no current in the circuit. This means that the capacitor is fully charged.

37-4 PROCEDURE

1. Connect the circuit as shown in Figure 6, using a $100 \text{ k}\Omega$ resistor and a $100 \text{ }\mu\text{F}$ capacitor (or close to these values). Note that the wire sticking out of **SW2** is not connected on the other side. This will be used later to discharge the capacitor.

2. Connect the Voltage Sensor set to measure Voltage and connect it to Capstone. In case voltage sensor is not available, use the Multimeter in Voltage mode.
3. The initial few steps are to familiarize you with how the capacitor behaves. Start with no voltage on the capacitor and the switch off. If there is remaining voltage on the capacitor, use a piece of wire to “short” the two leads together, draining any remaining charge. (Touch the ends of a wire to points **C5** and **C7** as shown in Figure 6 to discharge the capacitor.)
4. Now close the switch by pushing and holding the button down. Observe how the voltage across the capacitor changes with time. The voltage should rise as shown by ‘q’ in Fig 3.
5. If you now open the switch by releasing the button, the capacitor should remain at its present voltage with a very slow drop over time. This indicates that the charge you placed on the capacitor has no way to move back to neutralize the excess charges on the two plates. In practice, there is some leakage of current through the Voltage Sensor (or Multimeter), and the voltage will drop slowly across the capacitor.
6. Connect a wire between the points marked as **C5** and **C8** in the circuit, allowing the charge to drain back through the resistor. This can be done by connecting the wire sticking out of **SW2** into **C5**. Observe how the voltage across the capacitor changes with time. The voltage should fall off as shown by ‘q’ in Fig 5.
7. Repeat steps 3-5 until you have a good feeling for the process of charging and discharging of a capacitor through a resistance.
8. With the switch in ‘open’ position (i.e. not pressed), get the battery voltage by attaching the voltmeter prongs to the ends of the battery. This is the Battery EMF, or **V_{max}**.
9. Calculate the value of **0.632*V_{max}** and call this **V₁**. Calculate **0.368*V_{max}** and call this **V₂**.
10. Now attach the voltage sensor across the capacitor. Press ‘Record’ in Capstone to start measuring the voltage. Press the switch to start charging the capacitor and keep charging for a long time and note the maximum voltage that is reached across the capacitor. This should be the same as the battery EMF. If not, there is a leakage current through the voltmeter (since its resistance is not infinite). Use the measured maximum voltage as **V_{max}**.

If using the Multimeter, start the stopwatch and press the switch simultaneously, and note the time taken to reach **V₁**, i.e. **0.632*V_{max}**. Keep charging till the voltage changes no more (reaches **V_{max}**).

11. Taking the Data:

Taking the data by using voltage Sensor and Capstone:

- a) With the circuit connected as in Fig. 6, discharge the capacitor by momentarily connecting **C5** and **C7** with a piece of wire.
- b) Start Record in Capstone and press the switch to charge the capacitor. Fig 6.

- c) Keep charging the capacitor till it is 'fully charged' and reaches $V_{\max}$ (about $5 \cdot t_c$).
- d) Simultaneously release switch and connect the wire from **SW2** to **C5**. Fig 7.
- e) Stop recording when the voltage falls to about one tenth of $V_{\max}$.
- f) Use the Coordinates Tool in Capstone to determine the time taken to go from $V=0$ to $V=V_1$. This is the charging time t_c .
- g) Determine the time taken to go from $V_{\max}$ to V_2 . This is the Discharging Time t_d .
- h) Note the values of t_c and t_d in Table 1.

Taking the data by using Multimeter and Stopwatch:

- a) With the circuit connected as in Fig. 6, discharge the capacitor by momentarily connecting **C5** and **C7** by a wire.
- b) Start the stopwatch and press the switch simultaneously, and note the time taken to reach V_1 , i.e. $0.632 \cdot V_{\max}$. This is the charging time t_c .
- c) Turn off stopwatch. Keep charging the capacitor till it is 'fully charged' and reaches $V_{\max}$ (about $5 \cdot t_c$).
- d) Simultaneously release switch, connect the wire from **SW2** to **C5** and start the stopwatch. Note the time it takes to reach V_2 i.e. $0.368 V_{\max}$. Fig 7. This is the Discharging Time t_d .
- e) Stop recording.
- f) Note the values of t_c and t_d in Table 1.

12. Repeat the processes in 11) five times, and record in Table 1.

If the time to charge and/or discharge are less than about 5 seconds, or more than a few minutes, make sure you are using the correct procedure, or change the resistor or capacitor to a different value. For the next part, pick a second capacitor that is within about half to two times the first one. It should not be too much smaller or larger.

13. Add the second capacitor in series with the first one, to make the circuit as shown in figure 8. Repeat the measurement of charging and discharging time (i.e. step 11). Save the Capstone Screenshots and record the times in Table 2.
14. Now re-arrange the circuit to make it as shown in figure 9. You now have the two capacitors in parallel. Repeat the measurement of charging and discharging time (i.e. step 11). Save the Capstone screenshots and record the times in Table 2.

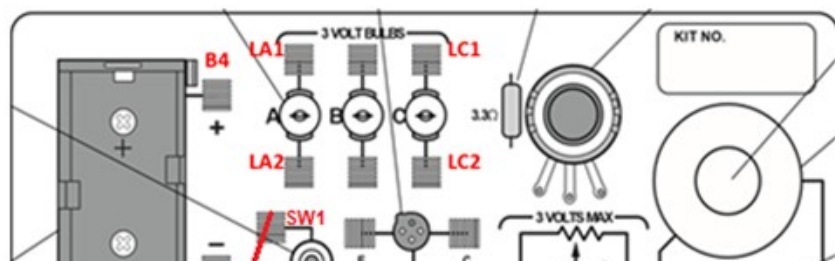


Figure 6: Single
Capacitor in R-C
Circuit.
Charging.

Figure 7: Single Capacitor in R-C
Circuit.
Dis-charging

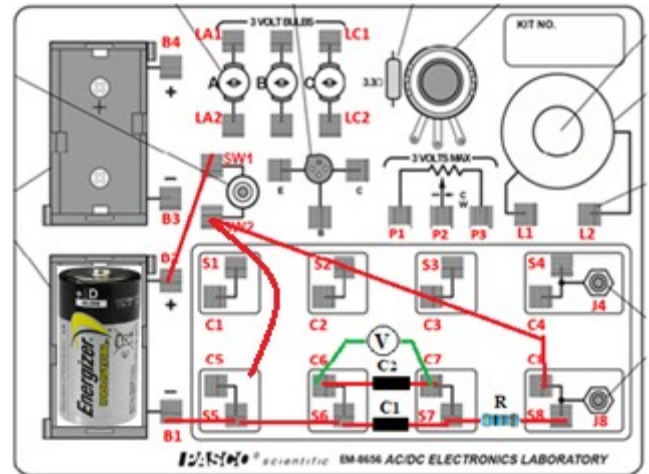
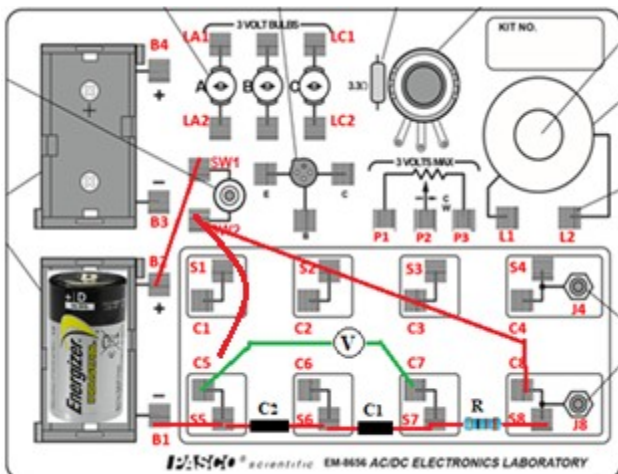
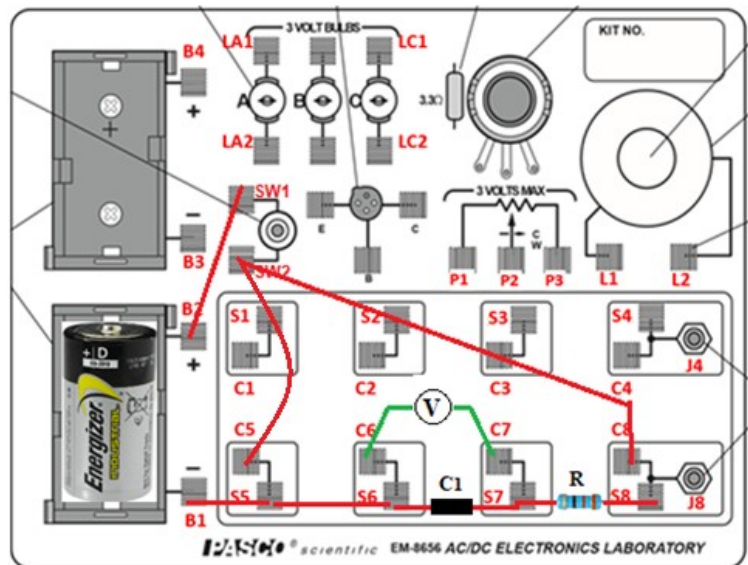


Figure 8: Capacitors in Series - charging

Figure 9: Capacitors in Parallel – charging

37-5 PRECAUTIONS

1. When using Capstone, you DO NOT have to press record and the switch at the same time. Press Record first, then press the switch.
2. When using the Multimeter, you DO HAVE to press the switch and start the stopwatch at the same time.
3. When discharging the capacitor, release the switch and connect the wire between switch and C5 at the same time.
4. Select the resistor and capacitors such the time period is not less than about ten seconds and not more than a few minutes.
5. When doing the series and parallel cases, the values of the two capacitors should be comparable to each other, i.e. one of them should be within 2 times the other in capacitance.

37-6 DATA: CAPACITORS IN CIRCUITS

Resistance: _____ Capacitance: _____ Time Constant $\tau = RC =$ _____

Battery potential: _____

Table 1: Time for charging and discharging a capacitor

Trial No.	Vmax V	V ₁ =0.632* Vmax V	V ₂ = 0.368 Vmax V	Measured Charging time t_c $0 - V_1$ s	Measured Discharging time t_d $V_{max} - V_2$ s	Percent error in time of charging	Percent error in time of discharging

Two Capacitors in Series and Parallel:

Resistance: _____

Capacitor 1: _____

Capacitor 2: _____

Table 2: Time for charging and discharging two capacitors in series and parallel.

Type of Circuit: Cap.s in:	Equiv. Cap. Ceq μF	Calc. time for t_c and t_d =RCeq s	Vmax v	V₁ =0.632* Vmax v	V₂ = 0.368 Vmax v	Meas. Charging time t_c s	Meas. Dis-charging time t_d s	Percent error in time of charging	Percent error in time of dis-charging
Series									
Parallel									

37-7 REPORT:

Upload the following in the DataSet for this Lab.

	<i>Take-Home Lab-Kit or In-Class if you are using Capstone.</i>	Points
1.	1 Show your circuit setup	5
2.	2 Completely filled up "Report Form". Make sure to include units.	20
3.	3 At least one Photograph of the circuit, showing voltage sensor in place for measurement	5
4.	4 At least two Capstone screenshots, one for charging and one for discharging the capacitor (select the "best" graphs and show the positions of t_c and t_d)	$2 \times 5 = 10$
5.	5 Sample calculations, one for charging time and one for discharging time	5
6.	6 Sources of Error in this experiment.	5
7.	7 Discussion of Results	10
	Total	60

	<i>In-Class if you are using the Multimeter and Stopwatch</i>	Points
1	Show your circuit setup	5
2	Completely filled up "Report Forms". Make sure to include units.	20
3	At least one Photograph of the circuit, showing multimeter in place for measurement	5
4	Sample calculations, one for Charging time and one for discharging time	5
5	Sources of Error in this experiment.	5
6	Discussion of Results	10
	Total	50

37-8 ADDITIONAL INFORMATION

RC Circuit

<https://www.khanacademy.org/science/electrical-engineering/ee-circuit-analysis-topic/ee-natural-and-forced-response/v/ee-rc-natural-response-intuition>

37-9 POINTS TO THINK ABOUT

1. Why are the times to charge and discharge the capacitor the same?
2. Why is the time to charge (and discharge) more for the parallel combination than for the series combination?
3. Why should the two capacitors be of comparable capacitance?

37-10 SAMPLE DATA

DATA: CAPACITORS IN CIRCUITS

Resistance: 99.5 k Ω Capacitance: 100 μ F Time Constant $\tau = RC = 9.95$ s

Battery potential: 1.620 V

Table 1: Time for charging and discharging a capacitor (see figure 10)

Trial No.	V _{max} V	V ₁ = 0.632* V _{max} V	V ₂ = 0.368 V _{max} V	Measured Charging time t _c 0 - V ₁ s	Measured Discharging time t _d V _{max} - V ₂ s	Percent error in time of charging	Percent error in time of discharging
1	1.450	0.9164	0.5336	14.30-3.70 = 10.6	78.5-67.75 = 10.75	6.5	8.0

$$100 * (10.6 - 9.95) / 9.95 = 6.5$$

$$100 * (10.75 - 9.95) / 9.95 = 8.0$$


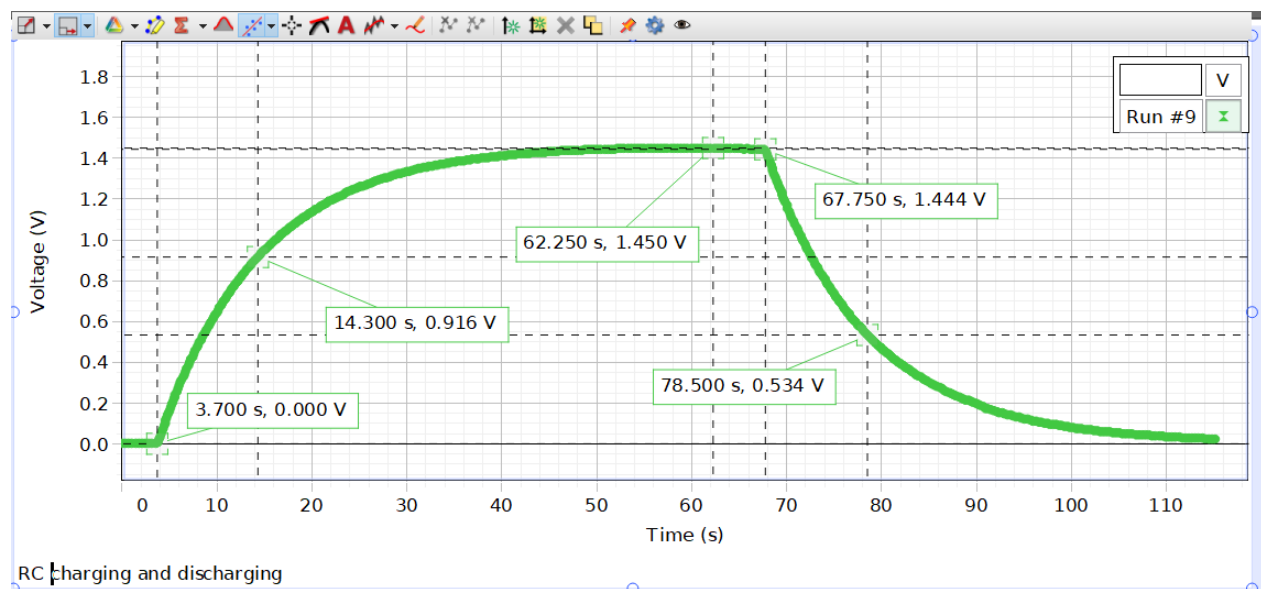


Figure 10: Single Capacitor

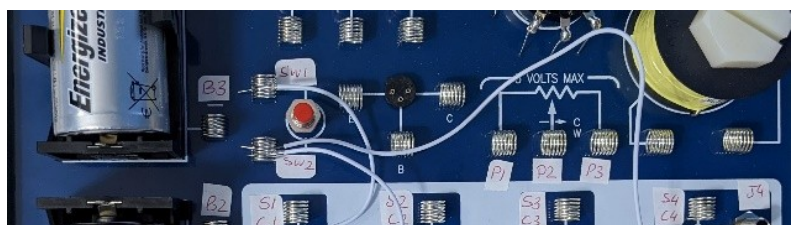

Two Capacitors in Series and Parallel:

Resistance: 99.5 kΩ

Capacitor 1: 100 μF

Capacitor 2: 47 μF

Table 2: Time for charging and discharging two capacitors in series and parallel.

Type of Circuit Cap.s in:	Equiv. Cap. Ceq μF	Calc. time for t_c and t_d =RCeq s	Vmax V	V₁ =0.632* Vmax V	V₂ = 0.368 Vmax V	Meas. Charging time t_c s	Meas. Discharging time t_d s	Percent error in time of charging	Percent error in time of discharging
Series Fig. 11	31.97	3.2 s	1.470	0.929	0.541	5.850-2.550= 3.30	32.850-29.500= 3.35	3.0	4.7
Parallel Fig. 12	147	14.7 s	1.272	0.804	0.468	15.750-3.400= 12.35	72.550-57.100= 15.45	16.3	5.1

Series: $1/C_{eq} = 1/C_1 + 1/C_2 = 1/100 + 1/47 = 0.031277$

$C_{eq} = 1/0.031277 = 31.97 \mu F$

Parallel: $C_{eq} = C_1 + C_2 = 100 + 47 = 147 \mu F$

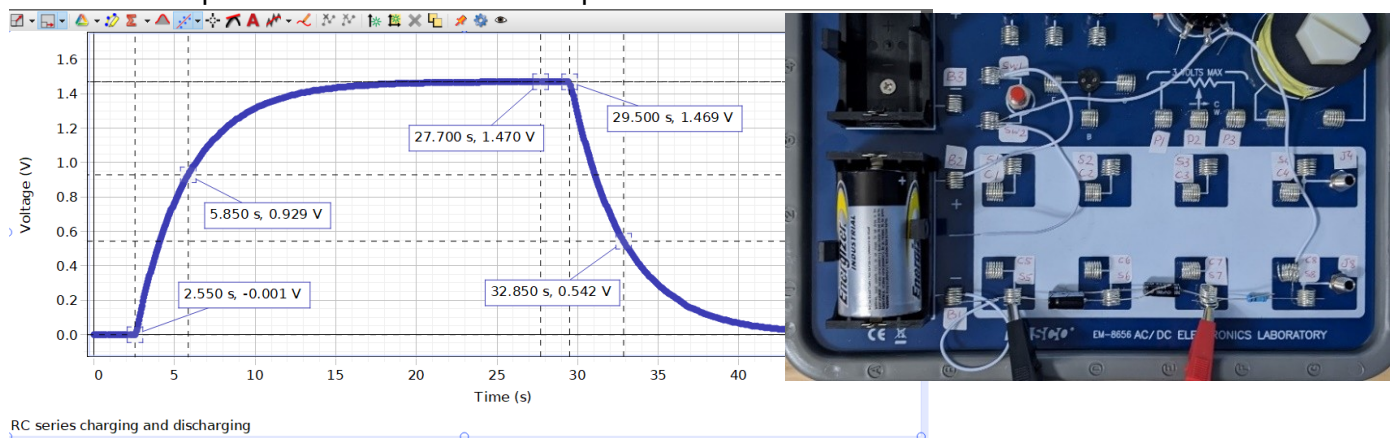


Figure 11: Two Capacitors in Series

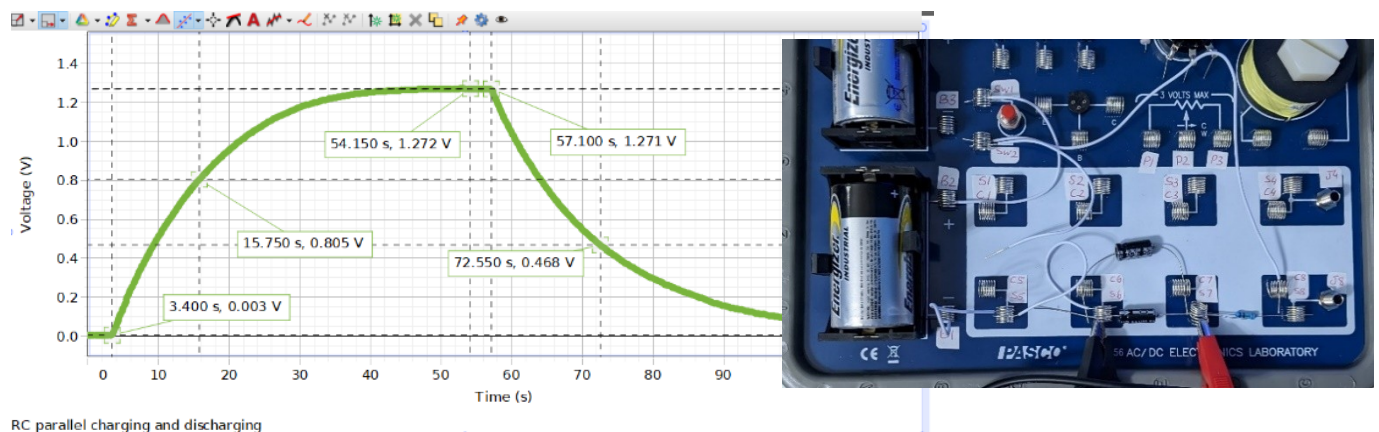


Figure 12: Two Capacitors in Parallel

Figure 13:
Single Capacitor

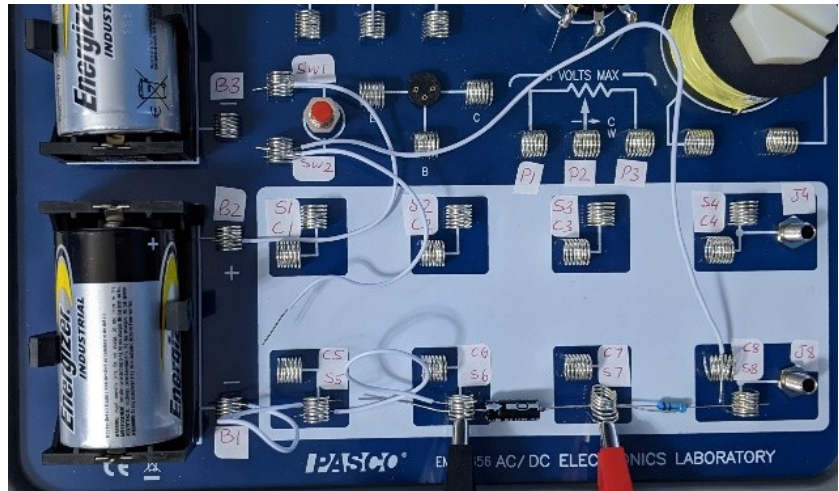


Figure 13B:
Two Capacitors in Series

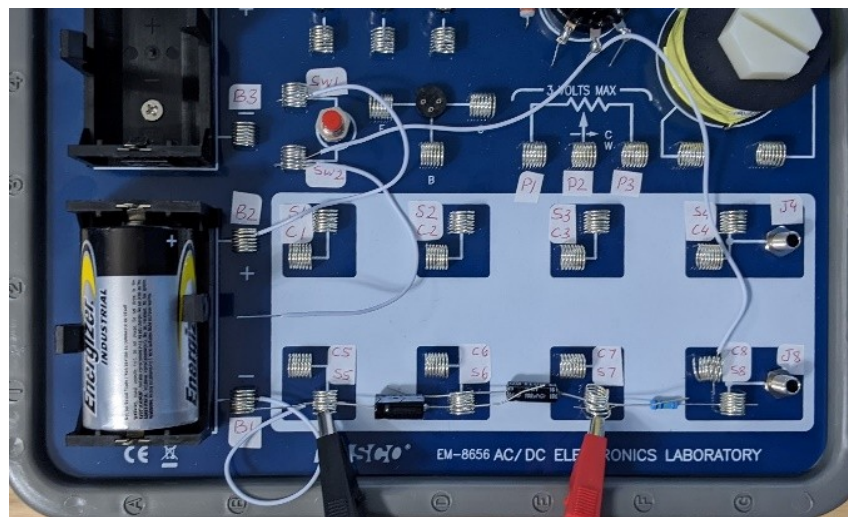


Figure 13C:
Two capacitors in parallel

