 


CHAPTER 3

Boolean Algebra and Digital Logic



Objectives

- Understand the relationship between Boolean logic and digital computer circuits.
- Learn how to design simple logic circuits.
- Understand how digital circuits work together to form complex computer systems.

3.1 Introduction (1 of 2)

- In the latter part of the nineteenth century, George Boole incensed philosophers and mathematicians alike when he suggested that logical thought could be represented through mathematical equations.
 - How dare anyone suggest that human thought could be encapsulated and manipulated like an algebraic formula?
- Computers, as we know them today, are implementations of Boole's *Laws of Thought*.
 - John Atanasoff and Claude Shannon were among the first to see this connection.

3.1 Introduction (2 of 2)

- In the middle of the twentieth century, computers were commonly known as “thinking machines” and “electronic brains.”
 - Many people were fearful of them.
- Nowadays, we rarely ponder the relationship between electronic digital computers and human logic. Computers are accepted as part of our lives.
 - Many people, however, are still fearful of them.
- In this chapter, you will learn the simplicity that constitutes the essence of the machine.

3.2 Boolean Algebra (1 of 17)

- Boolean algebra is a mathematical system for the manipulation of variables that can have one of two values.
 - In formal logic, these values are “true” and “false.”
 - In digital systems, these values are “on” and “off,” 1 and 0, or “high” and “low.”
- Boolean expressions are created by performing operations on Boolean variables.
 - Common Boolean operators include AND, OR, and NOT.

3.2 Boolean Algebra (2 of 17)

- A Boolean operator can be completely described using a truth table.
- The truth tables for the Boolean operators AND and OR are shown on the right.
- The AND operator is also known as a Boolean product. The OR operator is the Boolean sum.

X AND Y

X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X OR Y

X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

3.2 Boolean Algebra (3 of 17)

- The truth table for the Boolean NOT operator is shown on the right.
- The NOT operation is most often designated by a prime mark ($\mathbf{x'}$). It is sometimes indicated by an overbar ($\overline{\mathbf{x}}$) or an “elbow” ($\neg\mathbf{x}$).

NOT X	
X	X'
0	1
1	0

3.2 Boolean Algebra (4 of 17)

- A Boolean function has:
 - at least one Boolean variable,
 - at least one Boolean operator, and
 - at least one input from the set $\{0,1\}$.
- It produces an output that is also a member of the set $\{0,1\}$.

Now you know why the binary numbering system is so handy in digital systems.

3.2 Boolean Algebra (5 of 17)

- The truth table for the Boolean function:

$$F(x, y, z) = xz' + y$$

is shown on the right.

- To make evaluation of the Boolean function easier, the truth table contains extra (shaded) columns to hold evaluations of subparts of the function.

$$F(x, y, z) = xz' + y$$

x	y	z	z'	xz'	xz' + y
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

3.2 Boolean Algebra (6 of 17)

- As with common arithmetic, Boolean operations have rules of precedence.
- The NOT operator has the highest priority, followed by AND and then OR.
- This is how we choose the (shaded) function subparts in our table.

$$F(x, y, z) = xz' + y$$

x	y	z	z'	xz'	$xz' + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

3.2 Boolean Algebra (7 of 17)

- Digital computers contain circuits that implement Boolean functions.
- The simpler that we can make a Boolean function, the smaller the circuit that will result.
 - Simpler circuits are cheaper to build, consume less power, and run faster than complex circuits.
- With this in mind, we always want to reduce our Boolean functions to their simplest form.
- There are a number of Boolean identities that help us to do this.

3.2 Boolean Algebra (8 of 17)

- Most Boolean identities have an AND (product) form as well as an OR (sum) form. We give our identities using both forms. Our first group is rather intuitive:

Identity Name	AND Form	OR Form
Identity Law	$1x = x$	$0 + x = x$
Null Law	$0x = 0$	$1 + x = 1$
Idempotent Law	$xx = x$	$x + x = x$
Inverse Law	$xx' = 0$	$x + x' = 1$

3.2 Boolean Algebra (9 of 17)

- Our second group of Boolean identities should be familiar to you from your study of algebra:

Identity Name	AND Form	OR Form
Commutative Law	$xy = yx$	$x+y = y+x$
Associative Law	$(xy)z = x(yz)$	$(x+y)+z = x+(y+z)$
Distributive Law	$x+yz = (x+y)(x+z)$	$x(y+z) = xy+xz$

3.2 Boolean Algebra (10 of 17)

- Our last group of Boolean identities is perhaps the most useful.
- If you have studied set theory or formal logic, these laws are also familiar to you.

Identity Name	AND Form	OR Form
Absorption Law	$x(x+y) = x$	$x + xy = x$
DeMorgan's Law	$(xy) = x' + y'$	$(x+y)' = x'y'$
Double Complement Law	$(x)'' = x$	

3.2 Boolean Algebra (11 of 17)

- We can use Boolean identities to simplify:

$$F(x, y, z) = xy + x'z + yz$$

$$\begin{aligned} F(x, y, z) &= xy + x'z + yz \\ &= xy + x'z + yz(1) && \text{(Identity)} \\ &= xy + x'z + yz(x + x') && \text{(Inverse)} \\ &= xy + x'z + (yz)x + (yz)x' && \text{(Distributive)} \\ &= xy + x'z + x(yz) + x'(zy) && \text{(Commutative)} \\ &= xy + x'z + (xy)z + (x'z)y && \text{(Associative twice)} \\ &= xy + (xy)z + x'z + (x'z)y && \text{(Commutative)} \\ &= xy(1 + z) + x'z(1 + y) && \text{(Distributive)} \\ &= xy(1) + x'z(1) && \text{(Null)} \\ &= xy + x'z && \text{(Identity)} \end{aligned}$$

3.2 Boolean Algebra (12 of 17)

- Sometimes it is more economical to build a circuit using the complement of a function (and complementing its result) than it is to implement the function directly.
- DeMorgan's law provides an easy way of finding the complement of a Boolean function.
- Recall DeMorgan's law states:

$$(xy)' = x' + y' \quad \text{and} \quad (x + y)' = x'y'$$

3.2 Boolean Algebra (13 of 17)

- DeMorgan's law can be extended to any number of variables.
- Replace each variable by its complement and change all ANDs to ORs and all ORs to ANDs.
- Thus, we find the complement of:

$$F(x, y, z) = (xy) + (x'y) + (xz')$$

is:

$$\begin{aligned} F'(x, y, z) &= ((xy) + (x'y) + (xz'))' \\ &= (xy)' (x'y)' (xz')' \\ &= (x' + y') (x + y') (x' + z) \end{aligned}$$

3.2 Boolean Algebra (14 of 17)

- Through our exercises in simplifying Boolean expressions, we see that there are numerous ways of stating the same Boolean expression.
 - These “synonymous” forms are *logically equivalent*.
 - Logically equivalent expressions have identical truth tables.
- In order to eliminate as much confusion as possible, designers express Boolean functions in *standardized* or *canonical* form.

3.2 Boolean Algebra (15 of 17)

- There are two canonical forms for Boolean expressions: sum-of-products and product-of-sums.
 - Recall the Boolean product is the AND operation and the Boolean sum is the OR operation.
- In the sum-of-products form, ANDed variables are ORed together.
 - For example: $F(x, y, z) = xy + xz + yz$
- In the product-of-sums form, ORed variables are ANDed together.
 - For example: $F(x, y, z) = (x+y)(x+z)(y+z)$

3.2 Boolean Algebra (16 of 17)

- It is easy to convert a function to a sum-of-products form using its truth table.
- We are interested in the values of the variables that make the function true (= 1).
- Using the truth table, we list the values of the variables that result in a true function value.
- Each group of variables is then ORed together.

$$F(x, y, z) = xz' + y$$

x	y	z	$xz' + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

3.2 Boolean Algebra (17 of 17)

- The sum-of-products form for our function is:

$$F(x, y, z) = (x'yz') + (x'yz) + (xy'z') + (xyz') + (xyz)$$

$$F(x, y, z) = xz' + y$$

x	y	z	$xz' + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


We note that this function is not in simplest terms. Our aim is only to rewrite our function in canonical sum-of-products form.

3.3 Logic Gates (1 of 7)

- We have looked at Boolean functions in abstract terms.
- In this section, we see that Boolean functions are implemented in digital computer circuits called gates.
- A gate is an electronic device that produces a result based on two or more input values.
 - In reality, gates consist of one to six transistors, but digital designers think of them as a single unit.
 - Integrated circuits contain collections of gates suited to a particular purpose.

 3.3 Logic Gates (2 of 7)

- The three simplest gates are the AND, OR, and NOT gates.




- They correspond directly to their respective Boolean operations, as you can see by their truth tables.

3.3 Logic Gates (3 of 7)

- Another very useful gate is the exclusive OR (XOR) gate.
- The output of the XOR operation is true only when the values of the inputs differ.

X XOR Y		
X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

 

Note the special symbol
 $\oplus$
for the XOR operation.

3.3 Logic Gates (4 of 7)




- NAND and NOR are two very important gates. Their symbols and truth tables are shown on the right.

X NAND Y

X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

X NOR Y


X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

   


3.3 Logic Gates (5 of 7)

- NAND and NOR are known as *universal gates* because they are inexpensive to manufacture, and any Boolean function can be constructed using only NAND or only NOR gates.


AND

 

NOT

 


OR

 

 3.3 Logic Gates (6 of 7)

- Gates can have multiple inputs and more than one output.
 - A second output can be provided for the complement of the operation.
 - We'll see more of this later.



3.3 Logic Gates (7 of 7)

To determine the output of gates with multiple input gates, assuming n inputs:

- All n inputs must be 1 for the output of an AND gate to be 1.
- Only 1 of the n inputs must be 1 for the output of an OR gate to be 1.
- If any of the inputs are 0, the output of a NAND gate is 1.
- If all n inputs are 0, the output of a NOR gate is 1.
- If the number of inputs equal to 1 is odd, the output of an XOR gate is 1; otherwise, the output is 0.

3.4 Karnaugh Maps

- Simplification of Boolean functions leads to simpler (and usually faster) digital circuits.
- Simplifying Boolean functions using identities is time-consuming and error-prone.
- This special section presents an easy, systematic method for reducing Boolean expressions.

3.4.1 Introduction

- In 1953, Maurice Karnaugh was a telecommunications engineer at Bell Labs.
- While exploring the new field of digital logic and its application to the design of telephone circuits, he invented a graphical way of visualizing and then simplifying Boolean expressions.
- This graphical representation, now known as a Karnaugh map, or Kmap, is named in his honor.

3.4.2 Description of Kmaps and Terminology (1 of 5)

- A Kmap is a matrix consisting of rows and columns that represent the output values of a Boolean function.
- The output values placed in each cell are derived from the minterms of a Boolean function.
- A *minterm* is a product term that contains all of the function's variables exactly once, either complemented or not complemented.

3.4.2 Description of Kmaps and Terminology (2 of 5)

- For example, the minterms for a function having the inputs x and y are $x'y'$, $x'y$, xy' , and xy .
- Consider the Boolean function, $F(x, y) = xy + xy'$
- Its minterms are:

Minterm	x	y
$x'y'$	0	0
$x'y$	0	1
xy'	1	0
xy	1	1

3.4.2 Description of Kmaps and Terminology (3 of 5)

- Similarly, a function having three inputs, has the minterms that are shown in this diagram.

Minterm	x	y	z
$x'y'z'$	0	0	0
$x'y'z$	0	0	1
$x'yz'$	0	1	0
$x'yz$	0	1	1
$xy'z'$	1	0	0
$xy'z$	1	0	1
xyz'	1	1	0
xyz	1	1	1

3.4.2 Description of Kmaps and Terminology (4 of 5)

- A Kmap has a cell for each minterm.
- This means that it has a cell for each line for the truth table of a function.
- The truth table for the function $F(x,y) = xy$ is shown on the right along with its corresponding Kmap.

x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

$x \backslash y$	0	1
0	0	0
1	0	1

3.4.2 Description of Kmaps and Terminology (5 of 5)

- As another example, we give the truth table and Kmap for the function, $F(x,y) = x + y$ on the right.
- This function is equivalent to the OR of all of the minterms that have a value of 1. Thus:

$$F(x, y) = x + y = x'y + xy' + xy$$

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

		y	
		0	1
x	0	0	1
	1	1	1

3.4.3 Kmap Simplification for Two Variables (1 of 3)

- Of course, the minterm function that we derived from our Kmap was not in simplest terms.
 - That's what we started with in this example.
- We can, however, reduce our complicated expression to its simplest terms by finding adjacent 1s in the Kmap that can be collected into groups that are powers of two.
- In our example, we have two such groups.
 - Can you find them?

		y	
		0	1
x	0	0	1
	1	1	1

3.4.3 Kmap Simplification for Two Variables (2 of 3)

- The best way of selecting two groups of 1s from our simple Kmap is shown on the right.
- We see that both groups are powers of two and that the groups overlap.
- The next slide gives guidance for selecting Kmap groups.

		y	
		0	1
x	0	0	1
	1	1	1

3.4.3 Kmap Simplification for Two Variables (3 of 3)

- The rules of Kmap simplification are:
 - Groupings can contain only 1s; no 0s.
 - Groups can be formed only at right angles; diagonal groups are not allowed.
 - The number of 1s in a group must be a power of 2—even if it contains a single 1.
 - The groups must be made as large as possible.
 - Groups can overlap and wrap around the sides of the Kmap.

3.4.4 Kmap Simplification for Three Variables (1 of 7)

- A Kmap for three variables is constructed as shown in the diagram below.
- We have placed each minterm in the cell that will hold its value.
 - Notice that the values for the yz combination at the top of the matrix form a pattern that is not a normal binary sequence.

		yz			
		00	01	11	10
x	0	$X'Y'Z'$	$X'Y'Z$	$X'YZ$	$X'YZ'$
	1	$XY'Z'$	$XY'Z$	XYZ	XYZ'

3.4.4 Kmap Simplification for Three Variables (2 of 7)

- Thus, the first row of the Kmap contains all minterms where x has a value of zero.
- The first column contains all minterms where y and z both have a value of zero.

$x \backslash yz$					
		00	01	11	10
0	$X'Y'Z'$	$X'Y'Z$	$X'YZ$	$X'YZ'$	
1	$XY'Z'$	$XY'Z$	XYZ	XYZ'	

3.4.4 Kmap Simplification for Three Variables (3 of 7)

- Consider the function:

$$F(X, Y, Z) = X'Y'Z + X'YZ + XY'Z + XYZ$$

- Its Kmap is given below.
 - What is the largest group of 1s that is a power of 2?

		yz			
		00	01	11	10
x	0	0	1	1	0
	1	0	1	1	0

3.4.4 Kmap Simplification for Three Variables (4 of 7)

- This grouping tells us that changes in the variables x and y have no influence upon the value of the function: They are irrelevant.

x \ yz	00	01	11	10
	0	1	1	0
1	0	1	1	0

- This means that the function,

$$F(X, Y, Z) = X'Y'Z + X'YZ + XY'Z + XYZ$$

reduces to $F(x) = z$.

You could verify this reduction with
identities or a truth table.

3.4.4 Kmap Simplification for Three Variables (5 of 7)

- Now for a more complicated Kmap. Consider the function:

$$F(X, Y, Z) = X'Y'Z' + X'Y'Z + X'YZ \\ + X'YZ' + XY'Z' + XYZ'$$

- Its Kmap is shown below. There are (only) two groupings of 1s.
 - Can you find them?

		yz			
		00	01	11	10
x	0	1	1	1	1
	1	1	0	0	1

3.4.4 Kmap Simplification for Three Variables (6 of 7)

- In this Kmap, we see an example of a group that wraps around the sides of a Kmap.
- This group tells us that the values of x and y are not relevant to the term of the function that is encompassed by the group.
 - What does this tell us about this term of the function?

What about the 1s in the top row?

		yz			
		00	01	11	10
x	0	1	1	1	1
	1	1	0	0	1

3.4.4 Kmap Simplification for Three Variables (7 of 7)

- The 1s in the top row tell us that only the value of x is significant in that group.
- We see that it is complemented in that row, so the other term of the reduced function is $\mathbf{X'}$.
- Our reduced function is $\mathbf{F(X,Y,Z) = X' + Z'}$.

Recall that we had six minterms in our original function!

		yz			
		00	01	11	10
x	0	1	1	1	1
	1	1	0	0	1

3.4.5 Kmap Simplification for Four Variables (1 of 4)

- Our model can be extended to accommodate the 16 minterms that are produced by a four-input function.
- This is the format for a 16-minterm Kmap:

		yz			
		00	01	11	10
wx	00	$W'X'Y'Z'$	$W'X'YZ$	$W'X'YZ$	$W'X'YZ'$
	01	$W'XY'Z'$	$W'XYZ$	$W'XYZ$	$W'XYZ'$
	11	$WXY'Z'$	$WXYZ$	$WXYZ$	$WXYZ'$
	10	$WX'Y'Z'$	$WX'YZ$	$WX'YZ$	$WX'YZ'$

3.4.5 Kmap Simplification for Four Variables (2 of 4)

- We have populated the Kmap shown below with the nonzero minterms from the function:

$$F(W, X, Y, Z) = W'X'Y'Z' + W'X'Y'Z + W'X'YZ' + W'XYZ' + WX'Y'Z' + WX'Y'Z + WX'YZ'$$

- Can you identify (only) three groups in this Kmap?


Recall that groups can overlap.

wx \ yz	yz			
	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

3.4.5 Kmap Simplification for Four Variables (3 of 4)

- Our three groups consist of:
 - Group 1 that wraps the top and bottom with four 1s
 - Group 2 that spans the corners and contains four 1s
 - Group 3 that contains only two 1s
- Thus, we have three terms in our final function:

$$F(W, X, Y, Z) = Y' + X'Z' + W'YZ'$$

 

3.4.5 Kmap Simplification for Four Variables (4 of 4)

- It is possible to have a choice as to how to pick groups within a Kmap while keeping the groups as large as possible.
- The (different) functions that result from the groupings below are logically equivalent.

		yz			
		00	01	11	10
wx	00	1		1	
	01	1		1	1
	11	1			
	10	1			

		yz			
		00	01	11	10
wx	00	1		1	
	01	1		1	1
	11	1			
	10	1			

3.4.6 Don't Care Conditions (1 of 5)

- Real circuits don't always need to have an output defined for every possible input.
 - For example, some calculator displays consist of 7-segment LEDs. These LEDs can display $2^7 - 1$ patterns, but only ten of them are useful.
- If a circuit is designed so that a particular set of inputs can never happen, we call this set of inputs a don't care condition.
- They are very helpful to us in Kmap circuit simplification.

3.4.6 Don't Care Conditions (2 of 5)

- In a Kmap, a “don't care” condition is identified by an X in the cell of the minterm(s) for the don't care inputs.
- In performing the simplification, we are free to include or ignore the X s when creating our groups.

3.4.6 Don't Care Conditions (3 of 5)

- In one grouping in the Kmap below, we have the function:

$$F(W, X, Y, Z) = W'Y' + YZ$$

		yz			
		00	01	11	10
wx	00	X	1	1	X
	01		X	1	
	11	X		1	
	10			1	

3.4.6 Don't Care Conditions (4 of 5)

- A different grouping gives us the function:

$$F(W, X, Y, Z) = W'Z + YZ$$

		yz			
		00	01	11	10
wx	00	X	1	1	X
	01		X	1	
	11	X		1	
	10			1	

3.4.6 Don't Care Conditions (5 of 5)

■ The truth table of:

$$F(W, X, Y, Z) = W'Y' + YZ$$

wx \ yz				
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

differs from the truth table of:

$$F(W, X, Y, Z) = W'Z + YZ$$

wx \ yz				
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

- However, the values for which they differ are the inputs for which we have don't care conditions.

3.4.7 Summary (1 of 2)


- Kmaps provide an easy graphical method of simplifying Boolean expressions.
- A Kmap is a matrix consisting of the outputs of the minterms of a Boolean function.
- In this section, we have discussed 2-, 3-, and 4-input Kmaps. This method can be extended to any number of inputs through the use of multiple tables.

3.4.7 Summary (2 of 2)

- Recapping the rules of Kmap simplification:
 - Groupings can contain only 1s; no 0s.
 - Groups can be formed only at right angles; diagonal groups are not allowed.
 - The number of 1s in a group must be a power of 2—even if it contains a single 1.
 - The groups must be made as large as possible.
 - Groups can overlap and wrap around the sides of the Kmap.
 - Use don't care conditions when you can.

 3.5 Digital Components (1 of 8)

- The main thing to remember is that combinations of gates implement Boolean functions.




- The circuit below implements the Boolean function $F(x, y, z) = x + y'z$:

We simplify our Boolean expressions so that we can create simpler circuits.

 
3.5 Digital Components (2 of 8)

- Standard digital components are combined into single integrated circuit packages.
- Boolean logic can be used to implement the desired functions.




3.5 Digital Components (3 of 8)

- The Boolean circuit:


 


 - Can be rendered using only NAND gates as:



  3.5 Digital Components (4 of 8)

- So, we can wire the pre-packaged circuit to implement our function:



3.5 Digital Components (5 of 8)

- Boolean logic is used to solve practical problems.
- Expressed in terms of Boolean logic, practical problems can be expressed by truth tables.
- Truth tables can be readily rendered into Boolean logic circuits.

3.5 Digital Components (6 of 8)

- Suppose we are to design a logic circuit to determine the best time to plant a garden.
- We consider three factors (inputs):
 - (1) time, where 0 represents day and 1 represents evening;
 - (2) moon phase, where 0 represents not full and 1 represents full; and
 - (3) temperature, where 0 represents 45°F and below, and 1 represents over 45°F.
- We determine that the best time to plant a garden is during the evening with a full moon.

3.5 Digital Components (7 of 8)

- This results in the following truth table:


Time (x)	Moon (y)	Temperature (z)	Plant?
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

3.5 Digital Components (8 of 8)

- From the truth table, we derive the circuit:

Time (x)	Moon (y)	Temperature (z)	Plant?
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F(x,y,z) = xyz' + xyz = xy$$

 

3.6 Combinational Circuits (1 of 12)

- We have designed a circuit that implements the Boolean function:

$$F(X, Y, Z) = X + Y'Z$$

- This circuit is an example of *a combinational logic circuit*.
- Combinational logic circuits produce a specified output (almost) at the instant when input values are applied.
 - In a later section, we will explore circuits where this is not the case.


3.6 Combinational Circuits (2 of 12)

- Combinational logic circuits give us many useful devices.
- One of the simplest is the *half adder*, which finds the sum of two bits.
- We can gain some insight as to the construction of a half adder by looking at its truth table, shown on the right.

Inputs		Outputs	
x	y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 3.6 Combinational Circuits (3 of 12)

- As we see, the sum can be found using the XOR operation and the carry using the AND operation.



Inputs		Outputs	
x	y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


3.6 Combinational Circuits (4 of 12)

- We can change our half adder into a full adder by including gates for processing the carry bit.
- The truth table for a full adder is shown on the right.

Inputs			Outputs	
x	y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 3.6 Combinational Circuits (5 of 12)


- How can we change the half adder shown below to make it a full adder?



Inputs			Outputs	
x	y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

3.6 Combinational Circuits (6 of 12)


- Here's our completed full adder.

 

Inputs			Outputs	
x	y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 3.6 Combinational Circuits (7 of 12)

- Just as we combined half adders to make a full adder, full adders can be connected in series.
- The carry bit “ripples” from one adder to the next; hence, this configuration is called a *ripple-carry adder*.




Today's systems employ more efficient adders.

3.6 Combinational Circuits (8 of 12)

- Decoders are another important type of combinational circuit.
- Among other things, they are useful in selecting a memory location according to a binary value placed on the address lines of a memory bus.
- Address decoders with n inputs can select any of 2^n locations.


This is a block diagram
for a decoder.

 

 3.6 Combinational Circuits (9 of 12)


- This is what a 2-to-4 decoder looks like on the inside.

If $x = 0$ and $y = 1$, which output line is enabled?



 
3.6 Combinational Circuits (10 of 12)

- A multiplexer does just the opposite of a decoder.
- It selects a single output from several inputs.
- The particular input chosen for output is determined by the value of the multiplexer's control lines.
- To be able to select among n inputs, $\log_2 n$ control lines are needed.
- This is a block diagram for a multiplexer.



 3.6 Combinational Circuits (11 of 12)

- This is what a 4-to-1 multiplexer looks like on the inside.




$S_0 = 1$ and $S_1 = 0$
If _____, which input is
transferred to the output?

 3.6 Combinational Circuits (12 of 12)

- This shifter moves the bits of a nibble one position to the left or right.

If $S = 0$, in which direction do the input bits shift?




3.7 Sequential Circuits (1 of 30)

- Combinational logic circuits are perfect for situations when we require the immediate application of a Boolean function to a set of inputs.
- There are other times, however, when we need a circuit to change its value with consideration to its current state as well as its inputs.
 - These circuits have to “remember” their current state.
- *Sequential logic circuits* provide this functionality for us.

 
3.7 Sequential Circuits (2 of 30)

- As the name implies, sequential logic circuits require a means by which events can be sequenced.
- State changes are controlled by clocks.
 - A “clock” is a special circuit that sends electrical pulses through a circuit.
- Clocks produce electrical waveforms such as the one shown below.



 
3.7 Sequential Circuits (4 of 30)

- Circuits that change state on the rising edge or falling edge of the clock pulse are called *edge-triggered*.
- *Level-triggered circuits* change state when the clock voltage reaches its highest or lowest level.




 
3.7 Sequential Circuits (5 of 30)

- To retain their state values, sequential circuits rely on *feedback*.
- Feedback in digital circuits occurs when output is looped back to the input.
- A simple example of this concept is shown below.
 - If Q is 0, it will always be 0; if it is 1, it will always be 1. Why?



  
3.7 Sequential Circuits (6 of 30)

- You can see how feedback works by examining the most basic sequential logic components, the SR flip-flop.
 - The “SR” stands for set/reset.
- The internals of an SR flip-flop are shown below, along with its block diagram.



 3.7 Sequential Circuits (7 of 30)

- The behavior of an SR flip-flop is described by a characteristic table.
- $Q(t)$ means the value of the output at time t . $Q(t + 1)$ is the value of Q after the next clock pulse.



S	R	$Q(t + 1)$
0	0	$Q(t)$ (No change)
0	1	0 (Reset to 0)
1	0	1 (Set to 1)
1	1	Undefined


3.7 Sequential Circuits (8 of 30)

- The SR flip-flop actually has three inputs: S, R, and its current output, Q.
- Thus, we can construct a truth table for this circuit, as shown on the right.
- Notice the two undefined values. When both S and R are 1, the SR flip-flop is unstable.

S	R	Present State Q(t)	Next State Q(t + 1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Undefined
1	1	1	Undefined

 
3.7 Sequential Circuits (9 of 30)

- If we can be sure that the inputs to an SR flip-flop will never both be 1, we will never have an unstable circuit. This may not always be the case.
- The SR flip-flop can be modified to provide a stable state when both inputs are 1.
- This modified flip-flop is called a JK flip-flop, shown on the right.



 3.7 Sequential Circuits (10 of 30)


- On the right, we see how an SR flip-flop can be modified to create a JK flip-flop.
- The characteristic table indicates that the flip-flop is stable for all inputs.



J	K	$Q(t + 1)$
0	0	$Q(t)$ (No change)
0	1	0 (Reset to 0)
1	0	1 (Set to 1)
1	1	$Q'(t)$

 3.7 Sequential Circuits (11 of 30)


- Another modification of the SR flip-flop is the D flip-flop, shown on the right with its characteristic table.
- You will notice that the output of the flip-flop remains the same during subsequent clock pulses. The output changes only when the value of D changes.



D	$Q(t + 1)$
0	0
1	1

 3.7 Sequential Circuits (12 of 30)

- The D flip-flop is the fundamental circuit of computer memory.
 - D flip-flops are usually illustrated using the block diagram shown below.
- The characteristic table for the D flip-flop is shown below.





D	$Q(t + 1)$
0	0
1	1

3.7 Sequential Circuits (13 of 30)

- The behavior of sequential circuits can be expressed using characteristic tables or finite state machines (FSMs).
 - FSMs consist of a set of nodes that hold the states of the machine and a set of arcs that connect the states.
- Moore and Mealy machines are two types of FSMs that are equivalent.
 - They differ only in how they express the outputs of the machine.
- Moore machines place outputs on each node, while Mealy machines present their outputs on the transitions.

 
 
3.7 Sequential Circuits (14 of 30)

- The behavior of a JK flip-flop is depicted below by a Moore machine (left) and a Mealy machine (right).



  
3.7 Sequential Circuits (15 of 30)

- Although the behavior of Moore and Mealy machines is identical, their implementations differ.
- This is our Moore machine.



 3.7 Sequential Circuits (16 of 30)


- Although the behavior of Moore and Mealy machines is identical, their implementations differ.
- This is our Mealy machine.



3.7 Sequential Circuits (17 of 30)


- It is difficult to express the complexities of actual implementations using only Moore and Mealy machines.
 - For one thing, they do not address the intricacies of timing very well.
 - Secondly, it is often the case that an interaction of numerous signals is required to advance a machine from one state to the next.
- For these reasons, Christopher Clare invented the algorithmic state machine (ASM).
- The next slide illustrates the components of an ASM.

3.7 Sequential Circuits (18 of 30)

 

3.7 Sequential Circuits (19 of 30)

- This is an ASM for a microwave oven.

 


3.7 Sequential Circuits (20 of 30)

- Sequential circuits are used anytime that we have a “stateful” application.
 - A stateful application is one where the next state of the machine depends on the current state of the machine and the input.
- A stateful application requires both combinational and sequential logic.
- The following slides provide several examples of circuits that fall into this category.
- Can you think of others?

 
3.7 Sequential Circuits (21 of 30)

- This illustration shows a 4-bit register consisting of D flip-flops. You will usually see its block diagram (below) instead.



 
3.7 Sequential Circuits (22 of 30)

- A binary counter is another example of a sequential circuit.
- The low-order bit is complemented at each clock pulse.
- Whenever it changes from 0 to 1, the next bit is complemented, and so on through the other flip-flops.



A larger memory configuration is shown on the next slide.

3.7 Sequential Circuits (23 of 30)

 


3.7 Sequential Circuits (24 of 30)

- Convolutional coding and decoding require sequential circuits.
- One important convolutional code is the $(2, 1)$ convolutional code that underlies the PRML code which is briefly described at the end of Chapter 2.
- A $(2, 1)$ convolutional code is so named because two symbols are output for every one symbol input.
- A convolutional encoder for PRML with its characteristic table is shown on the next slide.


3.7 Sequential Circuits (25 of 30)

Input A	Current State B C	Next State B C	Output
0	00	00	00
1	00	10	11
0	01	00	11
1	01	10	00
0	10	01	10
1	10	11	01
0	11	01	01
1	11	11	10

 

 3.7 Sequential Circuits (26 of 30)

- This is the Mealy machine for our encoder.




Input <i>A</i>	Current State <i>B C</i>	Next State <i>B C</i>	Output
0	00	00	00
1	00	10	11
0	01	00	11
1	01	10	00
0	10	01	10
1	10	11	01
0	11	01	01
1	11	11	10

 3.7 Sequential Circuits (27 of 30)

- The fact that there is a limited set of possible state transitions in the encoding process is crucial to the error-correcting capabilities of PRML.
- You can see by our Mealy machine for encoding that:


$$F(1101\ 0010) = 11\ 01\ 01\ 00\ 10\ 11\ 11\ 10$$



 3.7 Sequential Circuits (28 of 30)


- The decoding of our code is provided by inverting the inputs and outputs of the Mealy machine for the encoding process.
- You can see by our Mealy machine for decoding that:

$$F(11 \ 01 \ 01 \ 00 \ 10 \ 11 \ 11 \ 10) = 1101 \ 0010$$



 3.7 Sequential Circuits (29 of 30)


- Yet another way of looking at the decoding process is through a lattice diagram.
- Here we have plotted the state transitions based on the input (top) and shown the output at the bottom for the string 00 10 11 11.



$$F(00 \ 10 \ 11 \ 11) = 1001$$

 3.7 Sequential Circuits (30 of 30)

- Suppose we receive the erroneous string: 10 10 11 11.
- Here we have plotted the accumulated errors based on the allowable transitions.
- The path of least error outputs is 1001, thus 1001 is the string of maximum likelihood.



$$F(00 \ 10 \ 11 \ 11) = 1001$$

3.8 Designing Circuits (1 of 3)

- We have seen digital circuits from two points of view: digital analysis and digital synthesis.
 - *Digital analysis* explores the relationship between a circuit's inputs and its outputs.
 - *Digital synthesis* creates logic diagrams using the values specified in a truth table.
- Digital systems designers must also be mindful of the physical behaviors of circuits including minute propagation delays that occur between the time when a circuit's inputs are energized and when the output is accurate and stable.

3.8 Designing Circuits (2 of 3)

- Digital designers rely on specialized software, such as VHDL and Verilog, to create efficient circuits.
 - Thus, software is an enabler for the construction of better hardware.
- Of course, software is, in reality, a collection of algorithms that could just as well be implemented in hardware.
 - Recall the Principle of Equivalence of Hardware and Software.

3.8 Designing Circuits (3 of 3)

- When we need to implement a simple, specialized algorithm and its execution speed must be as fast as possible, a hardware solution is often preferred.
- This is the idea behind *embedded systems*, which are small, special-purpose computers that we find in many everyday things.
- Embedded systems require special programming that demands an understanding of the operation of digital circuits, the basics of which you have learned in this chapter.

Conclusion (1 of 3)

- Computers are implementations of Boolean logic.
- Boolean functions are completely described by truth tables.
- Logic gates are small circuits that implement Boolean operators.
- The basic gates are AND, OR, and NOT.
 - The XOR gate is very useful in parity checkers and adders.
- The “universal gates” are NOR and NAND.

Conclusion (2 of 3)

- Computer circuits consist of combinational logic circuits and sequential logic circuits.
- Combinational circuits produce outputs (almost) immediately when their inputs change.
- Sequential circuits require clocks to control their changes of state.
- The basic sequential circuit unit is the flip-flop: The behaviors of the SR, JK, and D flip-flops are the most important to know.

Conclusion (3 of 3)

- The behavior of sequential circuits can be expressed using characteristic tables or through various finite state machines.
- Moore and Mealy machines are two finite state machines that model high-level circuit behavior.
- Algorithmic state machines are better than Moore and Mealy machines at expressing timing and complex signal interactions.
- Examples of sequential circuits include memory, counters, and Viterbi encoders and decoders.